

## حل التمرين 06

$$u - u_1 - u_2 - u_3 = 0 \Rightarrow \boxed{u_3 = u - u_1 - u_2}$$

$$u_3 = 6V$$

$$u_2 + u_1 + u_4 = 0 \Rightarrow \boxed{u_4 = -u_2 - u_1}$$

$$u_4 = -6V$$